

B.Sc Electronics III semester (CBCS) Pattern

Question bank for Practical Examination

1. a) Construct and study a half wave rectifier, also determine ripple factor.
b) Construct and study a full wave rectifier, also determine ripple factor.
c) Construct and study a bridge rectifier, also determine ripple factor.
2. a) Determine ripple factor of a full wave rectifier with series inductor filter.
b) Determine ripple factor of a full wave rectifier with shunt capacitor filter.
c) Determine ripple factor of a full wave rectifier with L-section filter.
d) Determine ripple factor of a full wave rectifier with π -section filter.
3. a) Study voltage regulator using IC-78XX.
b) Study voltage regulator using IC-79XX.
4. Construct a colpitt's oscillator and determine the frequency.
5. Construct a RC coupled phase shift oscillator and determine the frequency.
6. Determine time period and duty cycle of an Astable multivibrator.
7. a) Using simulation software construct a rectifier circuit.
b) Using simulation software construct a RC coupled amplifier and study the frequency response.
c) Using simulation software construct a Wien's bridge oscillator.
d) Using simulation software construct a Colpitt's oscillator.
e) Using simulation software construct a RC phase shift oscillator.
f) Using simulation software construct an Astable multivibrator.

G. Jalitha
CHAIRMAN BOS
Department of Physics
Telangana University
Nizamabad.